
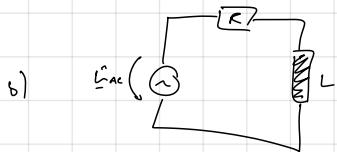


MHSZ - Übung

Übung 1

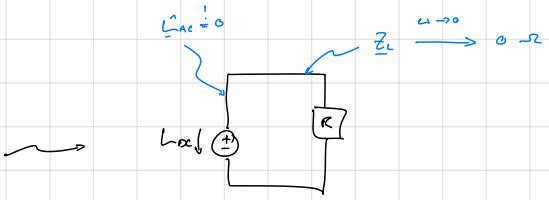a) $I_{DC} = \frac{U_{DC}}{R} = \frac{5V}{20\Omega} = 0.25A$



$$\hat{U}_{AC} = U_{AC} e^{j\frac{\pi}{2}}$$

$$Z = R + j\omega L$$

$$\hat{I}_{AC} = \frac{\hat{U}_{AC}}{Z} = \frac{\hat{U}_{AC} e^{j\frac{\pi}{2}}}{R + j\omega L}$$


$$\hat{I}_{AC} = \frac{\hat{U}_{AC} e^{-j\frac{\pi}{2}}}{R + j\omega L} = \frac{\hat{U}_{AC} e^{-j\frac{\pi}{2}}}{\sqrt{R^2 + (\omega L)^2} \cdot e^{j \arctan(\frac{\omega L}{R})}} = \frac{\hat{U}_{AC} e^{j[-\frac{\pi}{2} - \arctan(\frac{\omega L}{R})]}}{\sqrt{R^2 + (\omega L)^2}}$$

$$\rightarrow i_{AC}(t) = \frac{\hat{U}_{AC}}{\sqrt{R^2 + (\omega L)^2}} \cdot \cos \left[\omega t - \frac{\pi}{2} - \arctan \left(\frac{\omega L}{R} \right) \right] = 0.452A \cdot \sin(\omega t - 25.23)$$


c) $\rightarrow i(t) = i_{DC}(t) + i_{AC}(t) = 0.25 + \frac{\hat{U}_{AC}}{\sqrt{R^2 + (\omega L)^2}} \cdot \cos \left[\omega t - \frac{\pi}{2} - \arctan \left(\frac{\omega L}{R} \right) \right]$

MUSZ - WS09 : GSP 2

a)

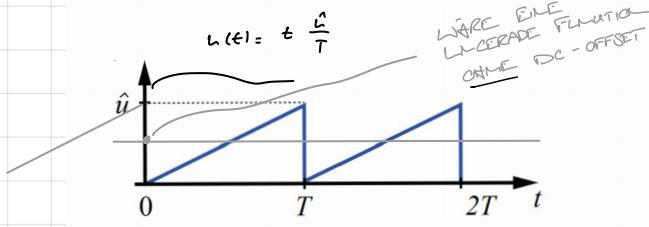

$a_n = 0 \quad \forall n \geq 1$
 $a_0 \neq 0 \iff$ WIR HABEN DA EINEN DC-OFFSET...

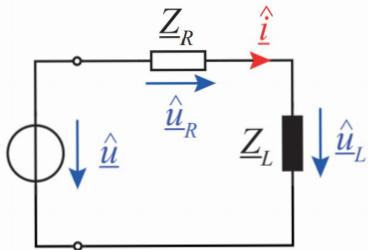

SCHART 1 : SAWTOOTH FORMULEN !!

$$\rightsquigarrow a_n = 0 \quad \forall n \geq 1$$

$$\rightsquigarrow a_0 = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \int_0^T t \frac{\hat{u}}{T} dt = \frac{\hat{u}}{T^2} \left[\frac{t^2}{2} \right]_0^T = \frac{\hat{u}}{2}$$

$$\rightsquigarrow b_n = \frac{2}{T} \int_0^T u(t) \sin\left(\frac{n\pi t}{T}\right) dt = \frac{2\hat{u}}{T^2} \int_0^T t \frac{\hat{u}}{T} \sin\left(\frac{n\pi t}{T}\right) dt = \frac{2\hat{u}}{T^2} \left(\left[\frac{-\hat{u}}{n\pi} t \cos\left(\frac{n\pi t}{T}\right) \right]_0^T + \int_0^T \frac{\hat{u}}{n\pi} \cos\left(\frac{n\pi t}{T}\right) dt \right) = \frac{2\hat{u}}{T^2} \frac{-\hat{u}}{n\pi} = \frac{-\hat{u}^2}{n\pi}$$

PARTIELL INTEGRIEREN...

→ IN FORMEL EINSETZEN :

(WOS-SIDES-REGEL)

$$u(t) = \frac{\hat{u}}{2} + \sum_{n=1}^{\infty} \frac{-\hat{u}}{n\pi} \sin(n\omega t)$$

b)

DC-TEIL : $I_{dc} = \frac{\frac{\hat{u}}{2}}{R} = \frac{\hat{u}}{2R}$

AC-TEIL : $\text{O - BE SPANNUNGSQUELLE} : u_n(t) = \frac{-\hat{u}}{n\pi} \cdot \cos(n\omega t - \frac{\pi}{2})$

KOT. BEZIEH $\hat{u}_n = \frac{-\hat{u}}{n\pi} e^{-j\frac{\pi}{2}}$

$\rightarrow Z = R + jn\omega L$

RESONANZ IST ALLE FREQUENZABSTANZEN

$$\rightarrow \hat{u}_n = \frac{\hat{u}_n}{Z} = \frac{\frac{-\hat{u}}{n\pi} e^{-j\frac{\pi}{2}}}{R + jn\omega L} = \frac{-\hat{u}}{n\pi \cdot \sqrt{R^2 + (n\omega L)^2}} \cdot e^{j\left[\frac{\pi}{2} - \arctan\left(\frac{n\omega L}{R}\right)\right]}$$

ZINTSEREKT : $u_n(t) = \frac{-\hat{u}}{n\pi \cdot \sqrt{R^2 + (n\omega L)^2}} \cdot \cos\left[n\omega t - \frac{\pi}{2} - \arctan\left(\frac{n\omega L}{R}\right)\right]$

ZUSAMMENSETTEN : $u(t) = I_{dc} + \sum_{n=1}^{\infty} u_n(t)$